
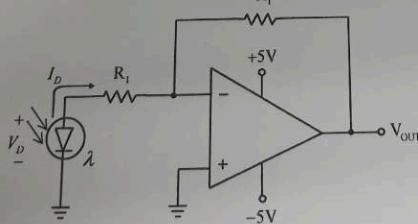


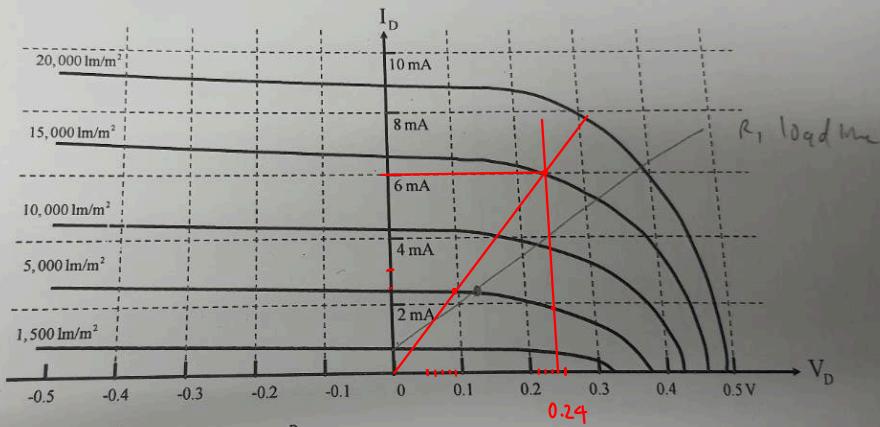



## 7. [10 points]

A photodiode with characteristics as shown in the given curves is connected to an inverting amplifier circuit with a voltage gain of -8 V/V as shown in the figure. The  $V_{out}$  becomes -1.92 V at a brightness of  $15,000 \text{ lm/m}^2$ . If the brightness is decreased by  $5,000 \text{ lm/m}^2$ , determine the output voltage, and the resistance of  $R_1$  and  $R_f$  for the amplifier.



Answer  $V_{out} = 1 \text{ V}$  (4 pts.)

$R_1 = 200 \Omega$  (3 pts.)

$R_f = 40 \Omega$  (3 pts.)

draw load line  
 $15,000 \text{ lm/m}^2$

①  $15,000 \text{ lm/m}^2$

$V_{out} = -1.92 \text{ V}$

$\Delta V = -8$

$A_V = V_{out}$

$-8 = \frac{-1.92}{V_{in}}$

$V_{in} = 0.24 \text{ V}$

เวลาที่สว่างกว่า 15,000 lm/m<sup>2</sup> มาก็จะได้ Vout ต่ำลง

จึง  $I_D = 6 \text{ mA}$

$I_D = V_D / R$

$6 \text{ mA} = 0.24 / R_1$

$R_1 = 40 \Omega$

$\therefore R_L = 40 \times 8 = 320 \Omega \rightarrow R_f$

$I = 2.4 \text{ mA}$

$V = 2.4 \text{ mA} \times 320 = 0.768 \text{ V}$

$V_{out} = 0 - 0.768 = -0.768 \text{ V}$

q1 ②  $5,000 \text{ lm/m}^2$

ให้  $I_D = 4 \text{ mA}$

$I = 4 \text{ mA}$

$V = 4 \text{ mA} \times 320 = 1.28 \text{ V}$

$V_{out} = 0 - 1.28 \text{ V} = -1.28 \text{ V}$

จึง  $I_D = 4 \text{ mA}$



8. [10 points]

Select only given components from the list below to implement a circuit that gets ac voltage signal (dc offset = 0) and gives the output as same (or almost the same) as the display of oscilloscope shown below. Circle around the selected components and write the circuit name (such as inverting amplifier, noninverting Schmitt trigger, integrator, lowpass filter, etc.) and draw the circuit diagram including the labels of Vin and Vout in the given area also.

**List of components**

- |                   |                   |                   |                   |
|-------------------|-------------------|-------------------|-------------------|
| a. R=15k $\Omega$ | b. R=33k $\Omega$ | c. R=43k $\Omega$ | d. R=68k $\Omega$ |
| e. C=220 pF       | f. C=270 pF       | g. C=470 pF       | h. OpAmp          |

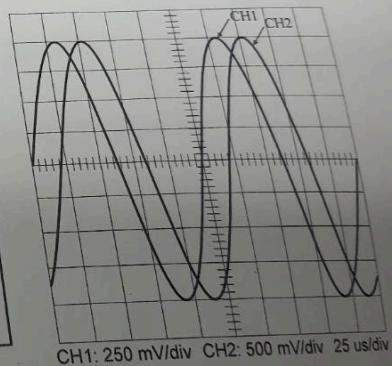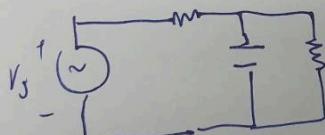Circuit diagram drawing area  
Circuit name = non inverting comp



$$Av = \frac{V_{out}}{V_{in}} = \frac{R}{\sqrt{R^2 + X_C^2}} = \frac{R}{2} = \frac{2000 \text{ mV}}{1000 \text{ mV}} = 2$$

**B: circuit analysis (w/ RC)**

$$V_{in} = 1000 \text{ mV}$$

$$\frac{360}{5} = 72$$

0

14.4

$$V_{out} = 2000 \text{ mV}$$

23.8

$$Av = 1 + \frac{V_{out}}{V_{in}}$$

$$\frac{72}{5} = 14.4$$

43.2

57.6 ~~8~~

$$f = 50$$

$$15k \quad 33k \quad 43k \quad 68k$$

$$Av = 1+2:3$$

72.0


$$\begin{array}{ll}
 C 220 \text{ pF} & X_C = 14468631.19 \quad 1.0367 \times 10^{-3} \quad 2.2807 \times 10^{-3} \quad 2.9719 \times 10^{-3} \quad 4.6997 \times 10^{-3} \\
 C 270 \text{ pF} & X_C = 11789255.04 \quad 1.2729 \times 10^{-3} \quad 2.7991 \times 10^{-3} \quad 3.6473 \times 10^{-3} \quad 5.7178 \times 10^{-3} \\
 C 470 \text{ pF} & X_C = 6772550.77 \quad 2.2148 \times 10^{-3} \quad 4.9725 \times 10^{-3} \quad 6.3499 \times 10^{-3} \quad 10.04 \times 10^{-3}
 \end{array}$$

## 5. [10 points]

The device of  $Z_x$  is connected to a bridge circuit that uses an ac voltage source  $V_s$  which can be adjusted both amplitude and frequency in range of 1 Vpp ~ 10 Vpp and 10 Hz ~ 10 kHz, respectively. Resistors  $R_1$  and  $R_2$  both are adjustable from  $100 \Omega \sim 20 \text{ k}\Omega$ . A resistor  $R_3$  is adjustable from  $1\text{k}\Omega \sim 10\text{k}\Omega$ . A capacitor is  $1 \mu\text{F}$  constant. Should the impedance  $Z_x$  be an **inductor** or a **capacitor** which measurable with this bridge circuit?

In the case that  $Z_x$  is an inductor, determine the minimum and maximum value of inductance and Q factor.

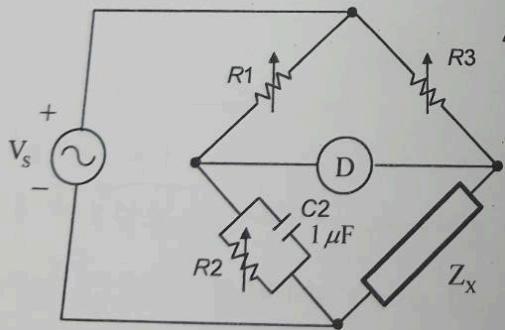In the case that  $Z_x$  is a capacitor, determine the minimum and maximum value of capacitance and D factor.



Answer  $Z_x$  is..... (2 pts.)  
and has .....ance with minimum of .....(2 pts.)  
and maximum of .....(2 pts.)  
and has ..... factor with minimum of .....(2 pts.)  
and maximum of .....(2 pts.)